

Introduction to Electrical & Electronics Circuits

**Course Code: EE
101**

Department: Electrical Engineering

Instructor Name: B.G. Fernandes

E-mail id: bgf @ee.iitb.ac.in



Sub Topics:

- Norton's theorem
- Source conversion
- Superposition theorem
- Time domain response of RL and RC circuit
 - Step response
 - Pulse response



Review

- Mesh current method

$$[R][I] = [V]$$

R – Known, V- Forcing function-known

I – to be determined

- Nodal Voltage method



$$[G][V] = [I]$$

G – Known, I- Forcing function-known


V – to be determined

⇒ Having determined [V],
branch

currents can be calculated

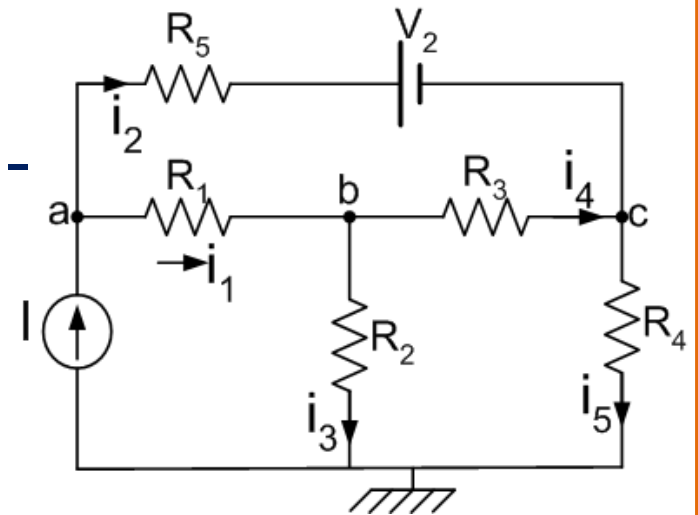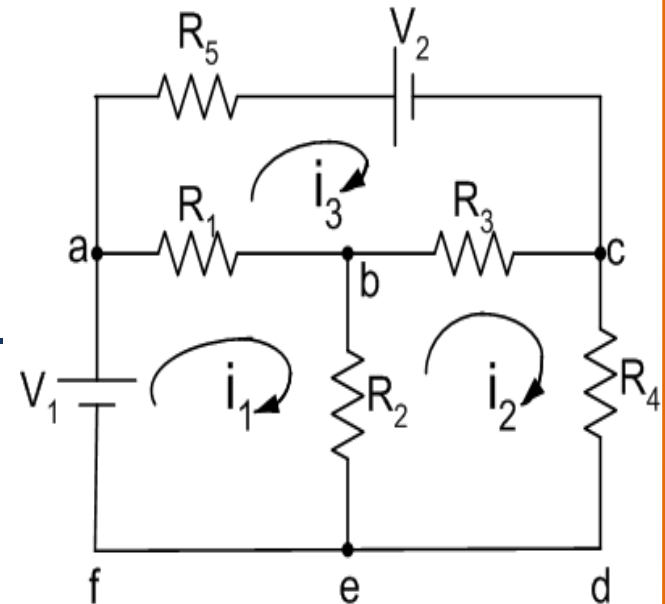


Thevenin's Theorem

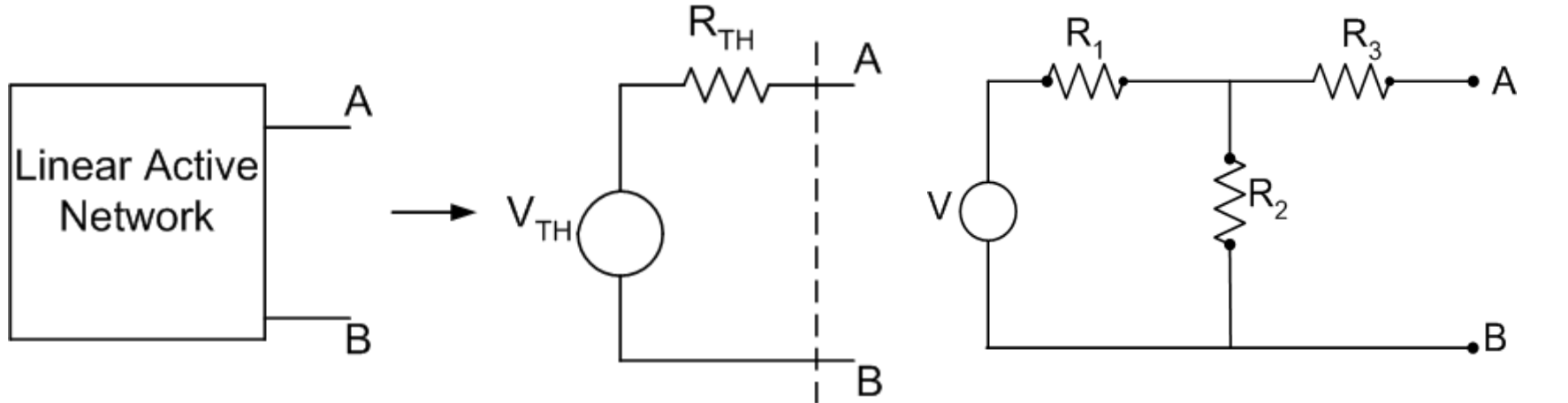


$$V_{TH} = \text{'V' across } R_2 \left(\frac{V}{R_1 + R_2} \right) R_2$$
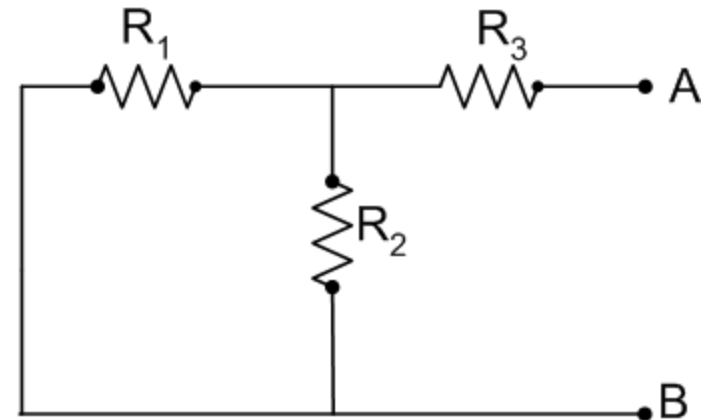
$$R_{TH} = R_3 + \frac{R_1 R_2}{R_1 + R_2} \quad i_L = \frac{V_{TH}}{R_{TH} + R}$$




Norton's Theorem:

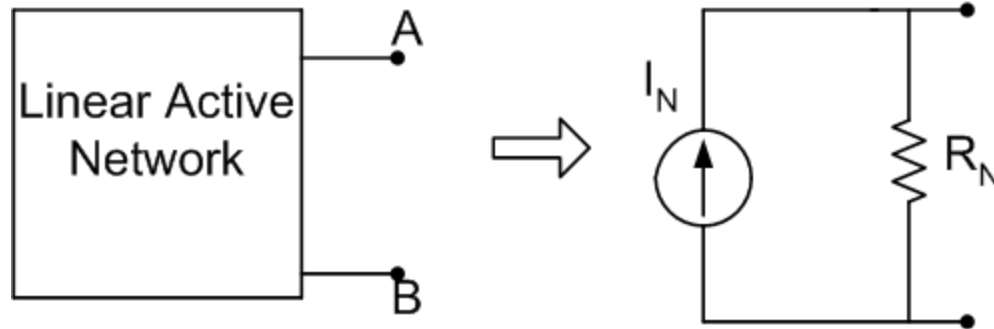


$I_N \rightarrow$ Current through the short circuit at the terminals

$$R_N = R_{TH}$$
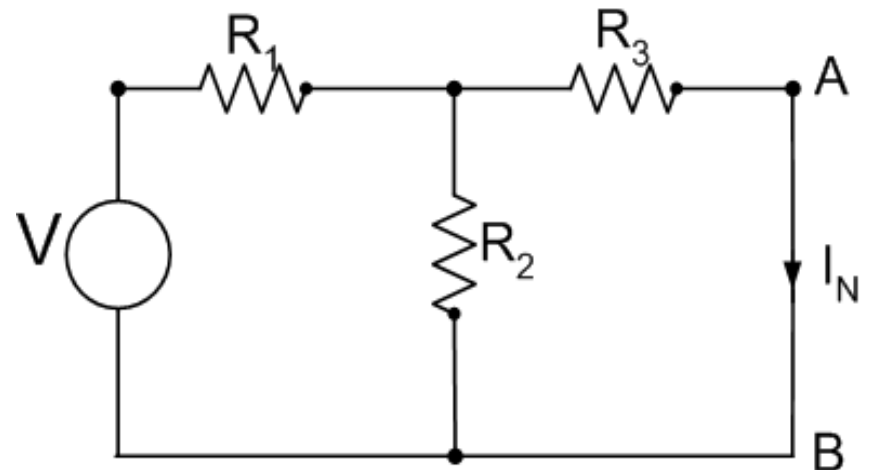
$$I_N = \frac{V}{\left(R_1 + \frac{R_2 R_3}{R_2 + R_3} \right)} \frac{R_2}{R_3 + R_2}$$



Source Conversion:

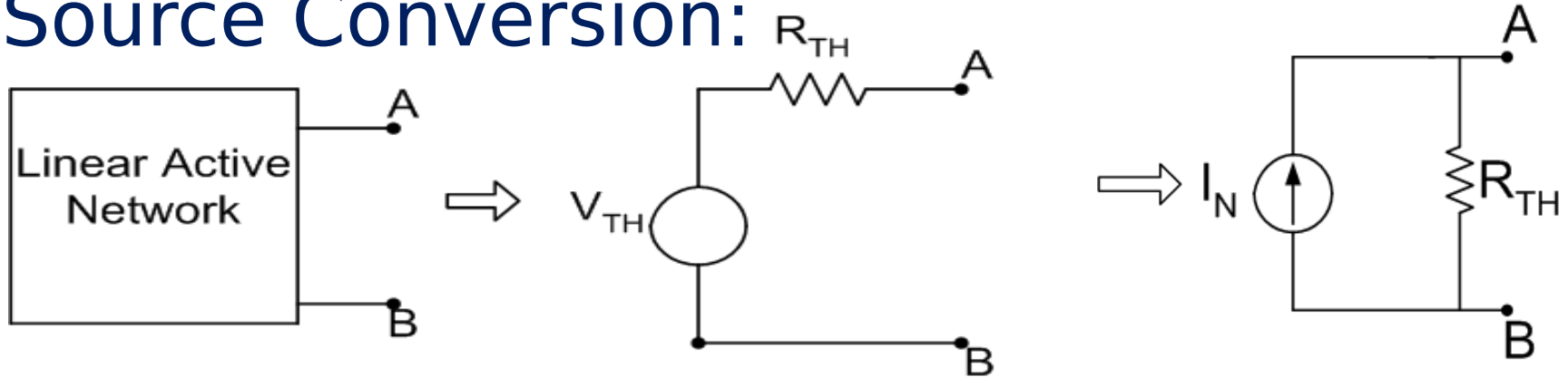

Short circuit the
terminals AB



Using Thevenin's theorem, $\frac{V_{TH}}{R_{TH}}$

From Norton's theorem, $I_{AB} = I_N$

$$\Rightarrow \frac{V_{TH}}{R_{TH}} = I_N \quad \therefore V_{TH} = I_N R_{TH}$$





e.g.:

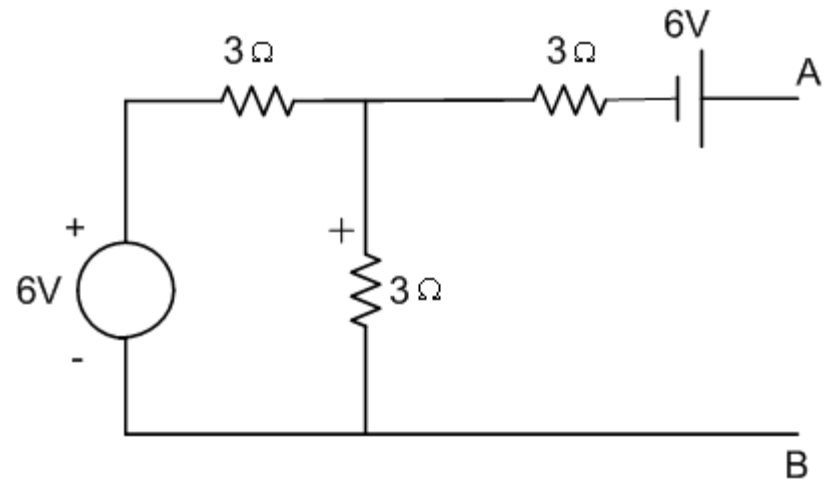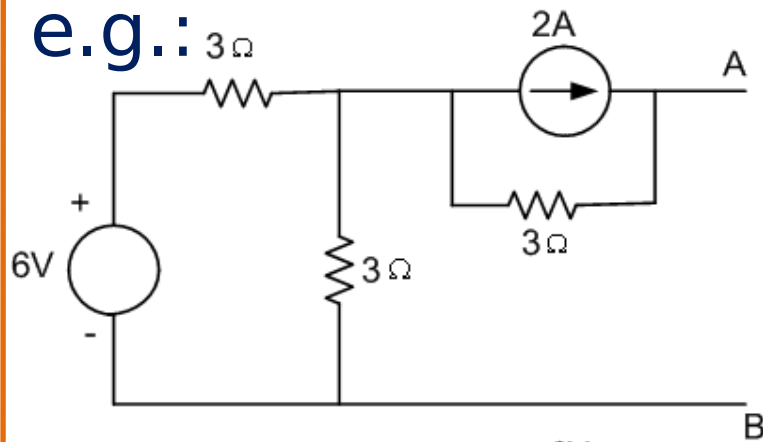

$$R_{TH} = 4.5\Omega$$


$$V_{TH} = \left(\frac{6}{6} \times 3\right) + 6 = 9V$$

$$I_{SC} = I_N = 2A$$

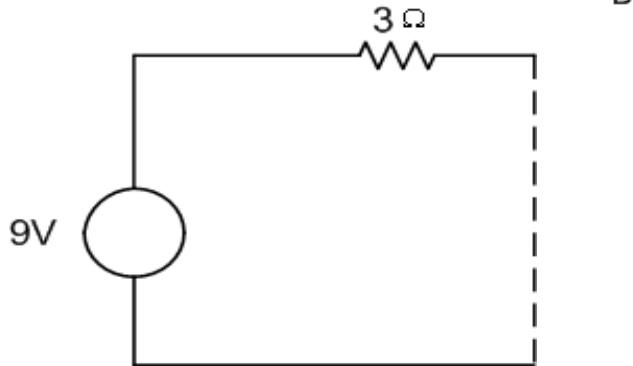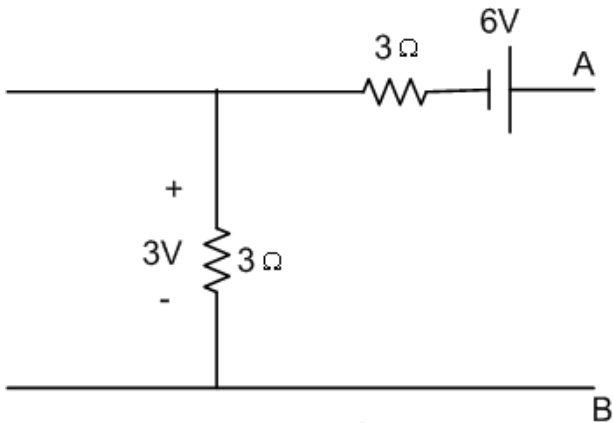

Circuit used for nodal analysis

e.g.

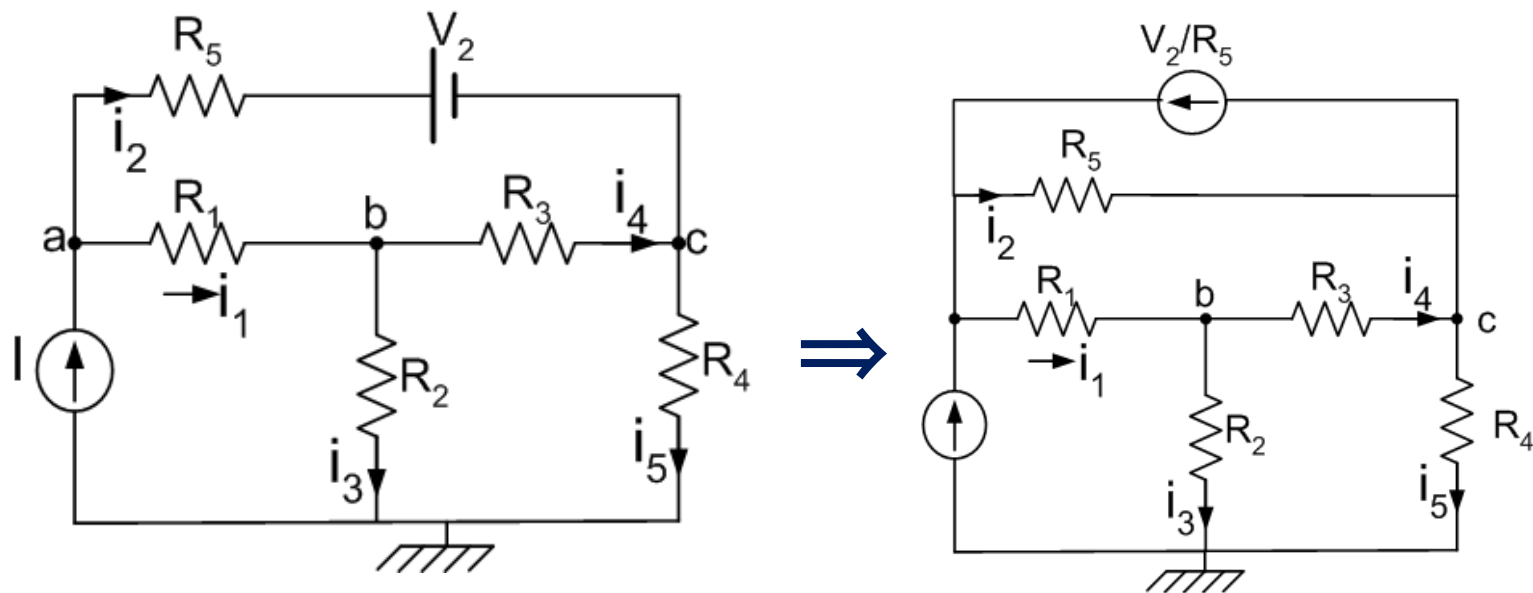

$$\begin{pmatrix} (G_1 + G_5) & -G_1 & -G_5 \\ -G_1 & (G_2 + G_3 + G_1) & -G_3 \\ -G_5 & -G_3 & (G_3 + G_4 + G_5) \end{pmatrix} \begin{pmatrix} v_a \\ v_b \\ v_c \end{pmatrix} = \begin{pmatrix} I + \frac{V_2}{R_5} \\ 0 \\ -\frac{V_2}{R_5} \end{pmatrix}$$



Equivalent circuit of a transistor amplifier:


Determine V_2 (V_{TH}) and R_{TH}

$$V_2 = -20 \times 10^3 \times 50i_1$$

$$2 \times 10^{-3} = 2 \times 10^3 i_1 + \frac{V_2}{5000}$$

$$\therefore i_1 = 1.11 \times 10^{-6} \text{ A}$$

$$\& V_2 = -1.11 \text{ V}$$

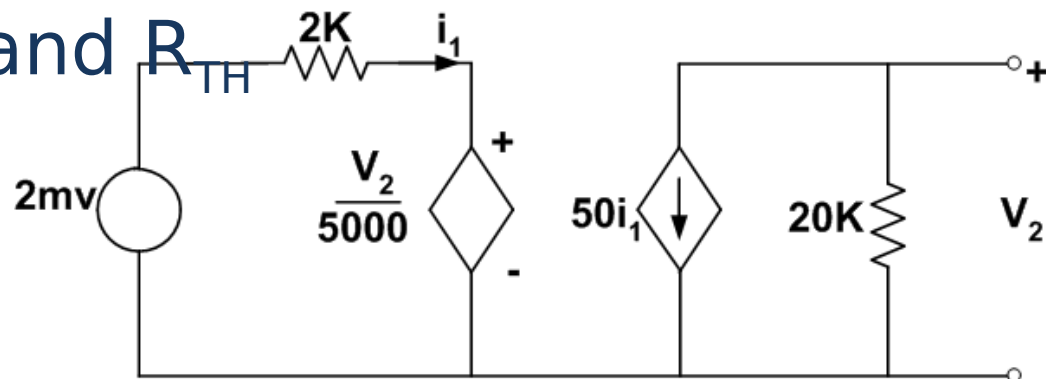

$$R_{TH} = \frac{V_{TH}}{i_{sc}}, i_{sc} |_{V_2=0} = -50i_1$$


$$2 \times 10^{-3} = 2 \times 10^3 \left(\frac{-i_{sc}}{50} \right)$$

$$\therefore i_{sc} = -50 \times 10^{-6}, \therefore R_{TH} = 22.2 \text{ k}\Omega$$



Superposition Theorem:

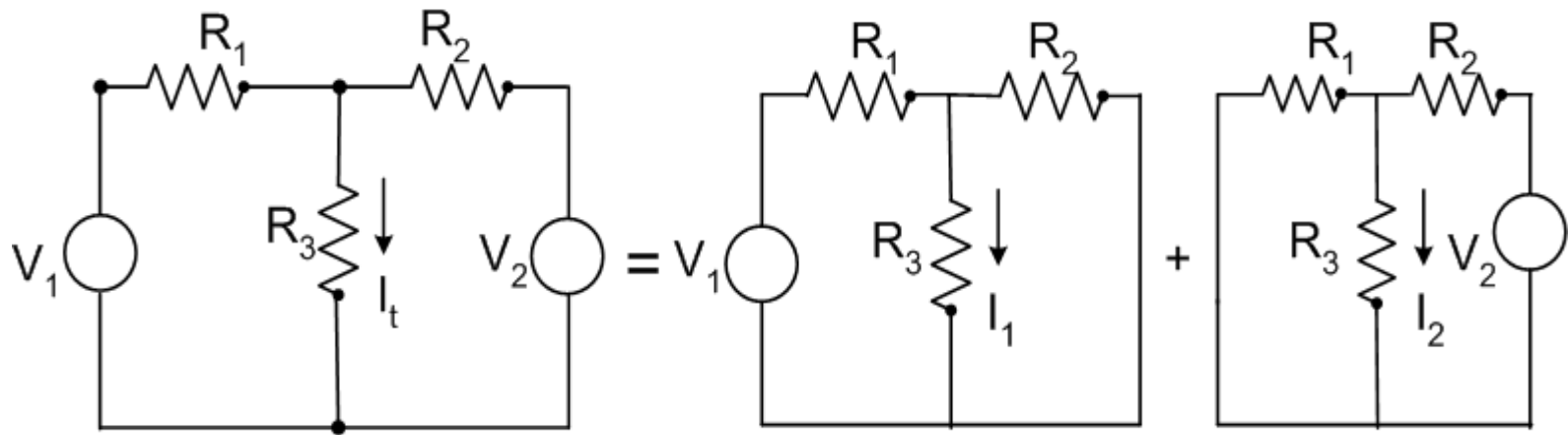The response in any element of linear network having two or more sources is the sum of responses obtained with each source acting separately, with all other sources set equal to zero.




$$I_t = I_1 + I_2$$

If $x_1 \rightarrow y_1$
& $x_2 \rightarrow y_2$

For a linear system, if $(x_1 \Rightarrow x_2) \Rightarrow (y_1 + y_2)$



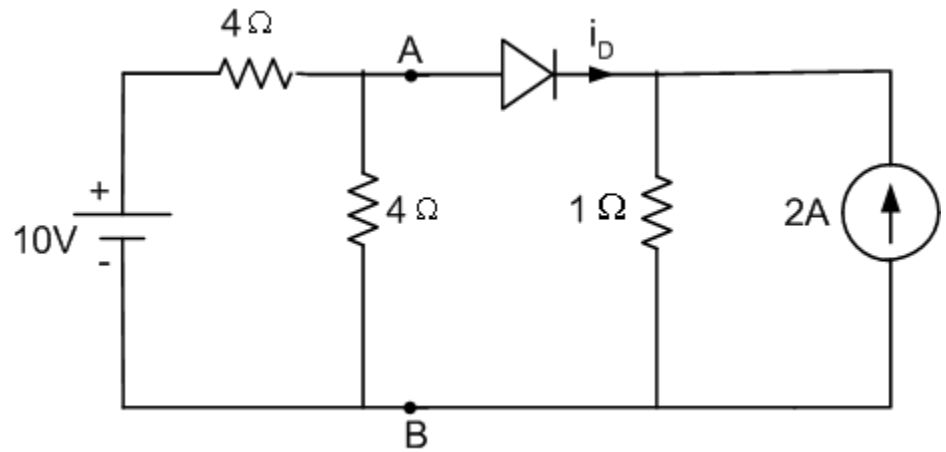Determine
(Assume diode is
ideal)
Circuit is non-
linear



'V' across $1\Omega = (2 + i_D)$

$$= V_{AB}$$

\therefore 'i' supplied by battery

$$= \frac{(2 + i_D)}{4} + i_D = \frac{5i_D + 2}{4}$$

Applying KVL

$$10 = \frac{5i_D + 2}{4} * 4 + (2 + i_D)$$

$$i_D = 1A$$




Time domain response of RC and RL circuits

- No transients in purely resistive circuit
- I cannot change instantaneously in an inductor
- V across a capacitor cannot change instantaneously

Step response: DC voltage or current suddenly applied to the circuit

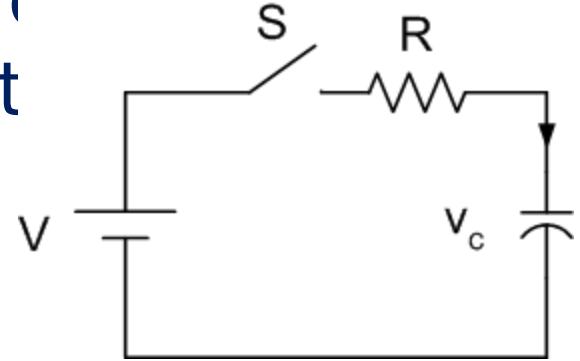RC circuit: $V_c = V_f + (V_{ci} - V_f)e^{-\frac{t}{\tau}}$



where, τ = Time constant

Circuit is assumed to attain steady state at $t = 5\tau$

V_{ci} = capacitor voltage at $t = 0$, V_f is the final value




Step response of R-C circuit

Case i)

$$v_c = 0 \text{ at } t = 0$$

$$v_c = 0 \text{ at } t = 0^+$$

$$V_R = V \text{ \& } i = \frac{V}{R}$$

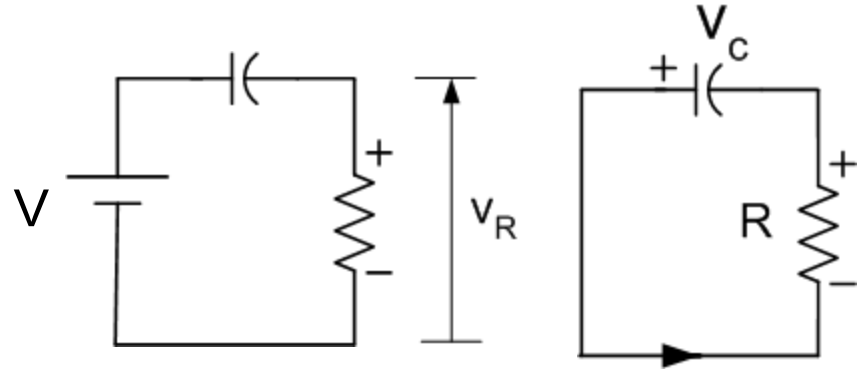

At steady state $v_c = V, I = 0 \therefore V_R = 0$


Steady state is attained at $t \approx T$

At $t = T^+$

$$v_R = -v_c \text{ \& } i = -\frac{v_c}{R} = \frac{-V_R}{R}$$

At steady state, v_c and $i = 0$.

Observation: 'i' through 'C' change instantaneously

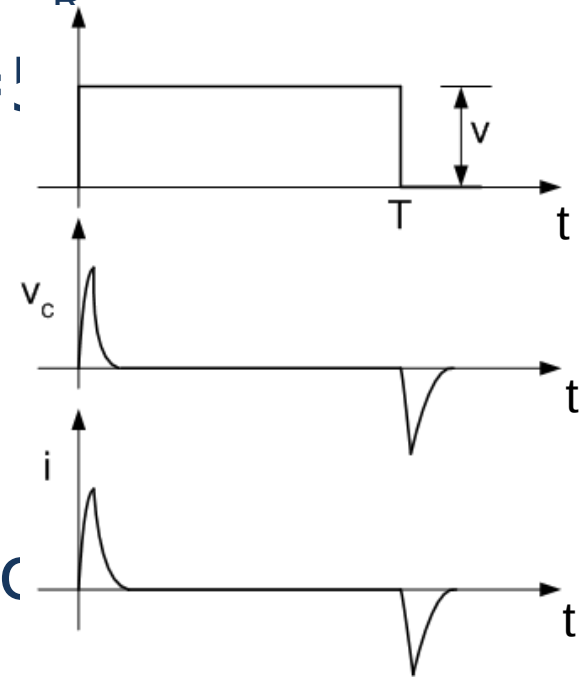


Case 2: $\tau \gg T$

V_c increases gradually
So, $|v_c|$ is a small fraction
of V at $t = T$.

Initial portion of v_c is linear
 $v_c \Rightarrow$ integral of V

\Rightarrow Integrator

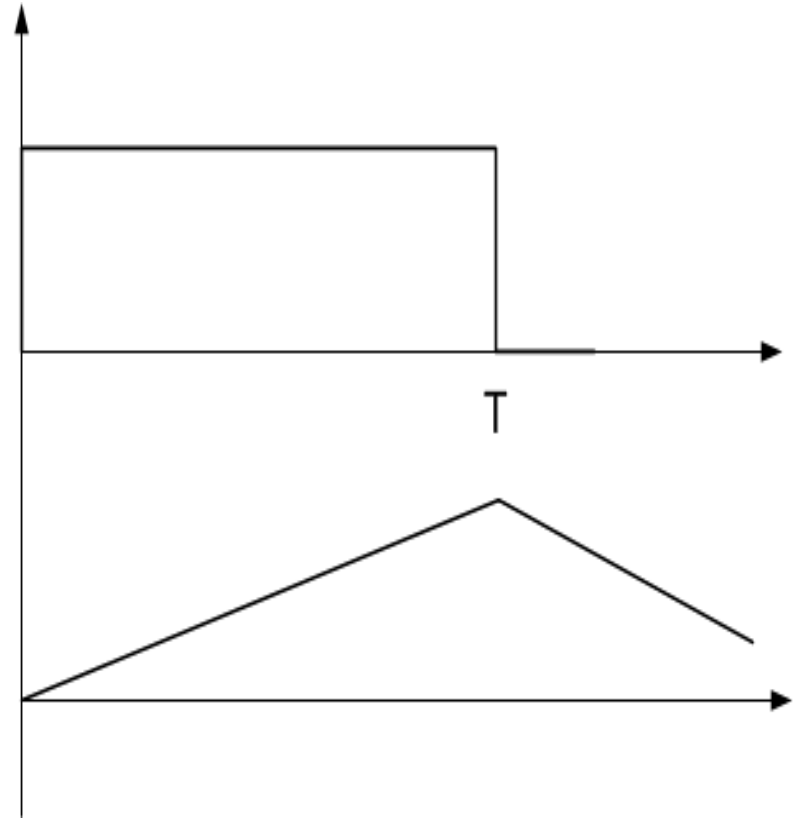


Step response of R-L circuit

'S' at 1:



$$V = iR + L \frac{di}{dt}$$
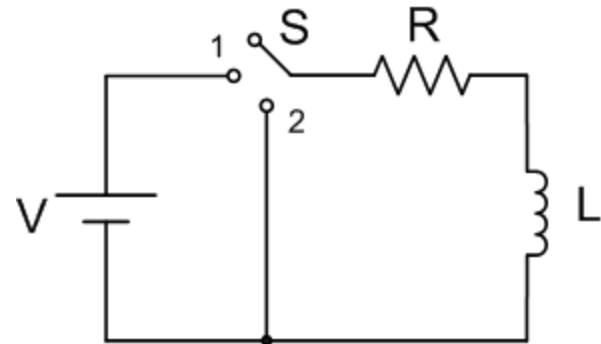
$$i_L = \frac{V}{R} \left(1 - e^{-\frac{t}{\tau}} \right)$$



'S' at 2: 'i' will decay
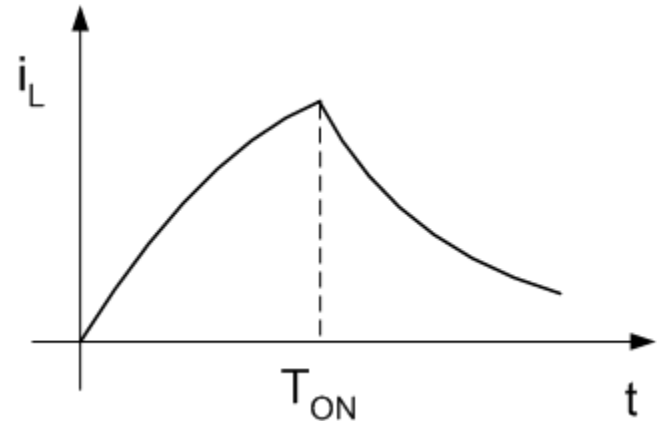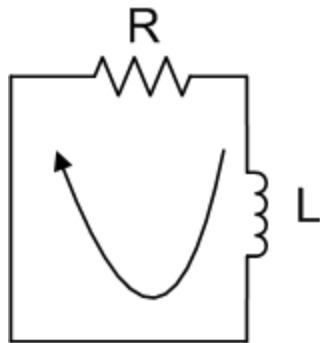
$$i_L = \frac{V}{R} e^{-\frac{t}{\tau}}$$




Step response of R-L circuit

$T ? \tau$

$i = 0$ at $t = 0$

$i = 0$ at $t = 0^+$

$$\therefore v_L = V$$

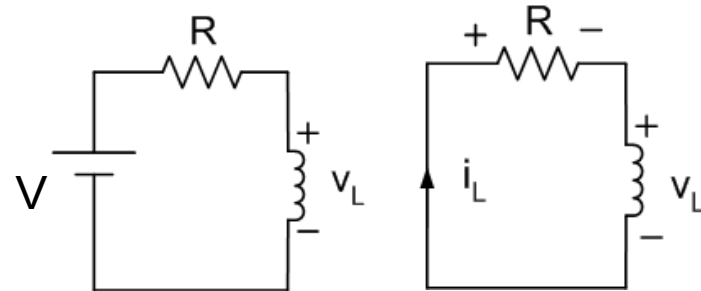


At steady state $\Rightarrow v_L = 0$

Steady state is attained at $t \approx$

At $t = T^+ V_L = 0, i = I, v_L = -IR$

\Rightarrow Differentiator


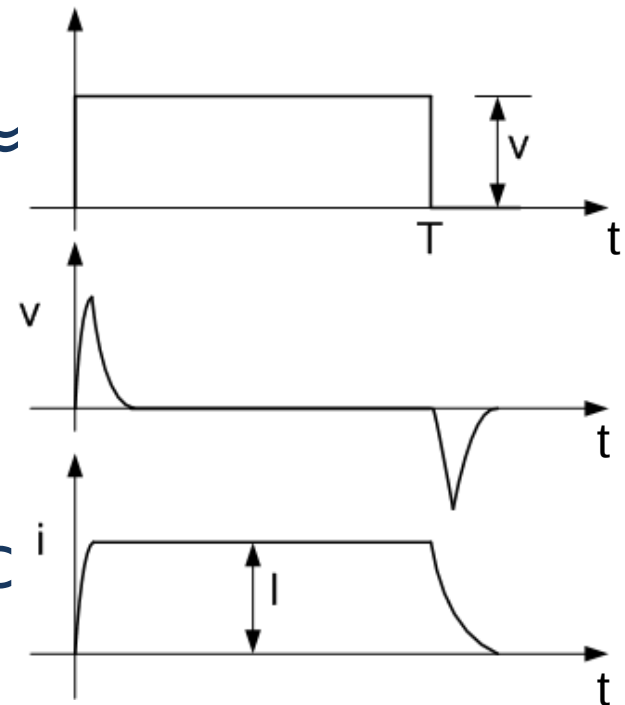
Observation: 'V' across 'L' changes instantaneously



Problem:

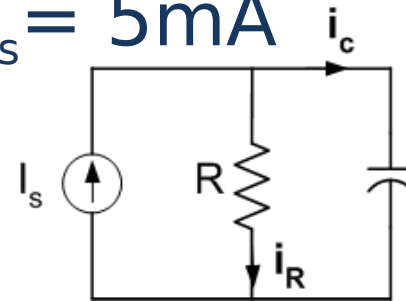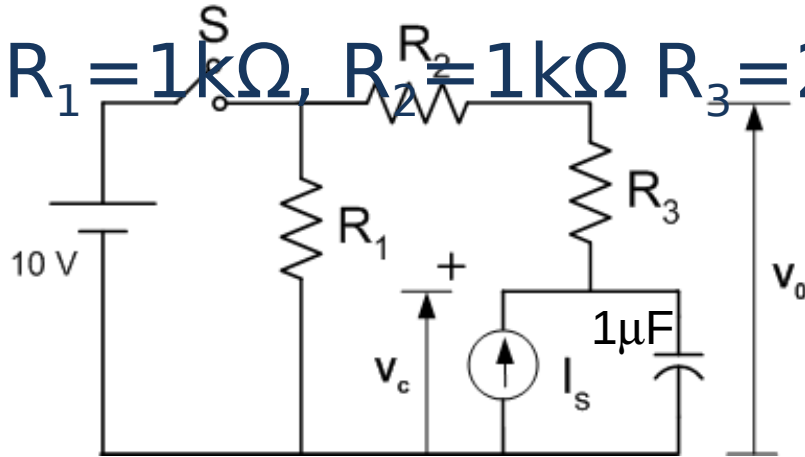a) 'S' is kept open for long time. 'S' is then closed at an instant of time considered to be $t = 0$ msec. Determine V_c & V_o at $t = 0^+$ if

$R_1 = 1k\Omega$, $R_2 = 1k\Omega$, $R_3 = 2k\Omega$ & $I_s = 5mA$



Eq circuit when S is open:

I_s charges 'C'

\therefore As $v_c \uparrow$, $i_R \uparrow$ & $\therefore i_c \downarrow$ $Q i_s = i_c + i_R$

\Rightarrow At Steady state when $i_c = 0$ & $i_R = 5mA$



$\therefore v_c$ when $i_c = 0$ is $5 \times 4 = 20V$



$$\therefore v_{c(t=0^-)} = 20V \text{ \&}$$


$$v_{o(t=0^-)} = 20 - 2 \times 5 = 10V$$

OR

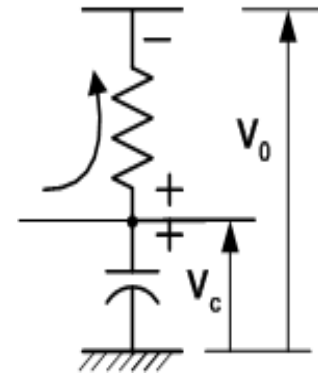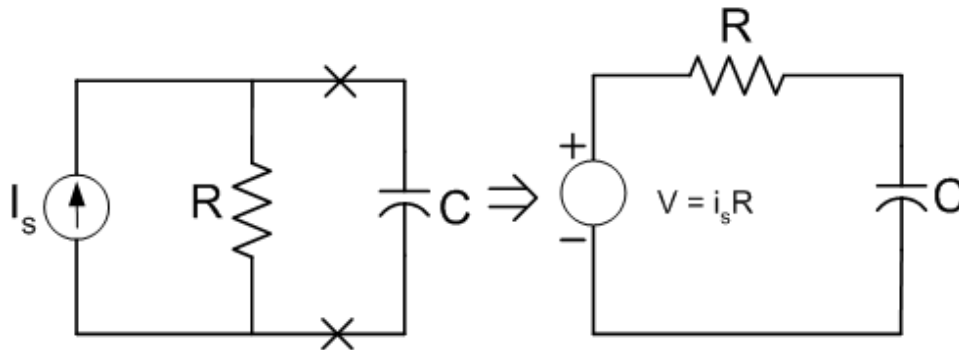

Steady state $V_c = V = i_c R$ and $\tau = RC$

V_o at $t = 0_+$?

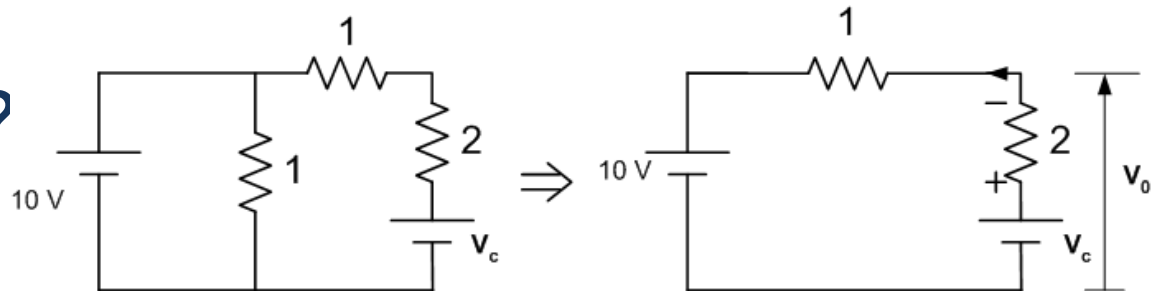


$$v_{c(0^-)} = v_{c(0^+)} = 20V$$

$$\therefore V_{o(0^+)} = 20 - \frac{(20-10) \times 2}{3} = 13.33V$$



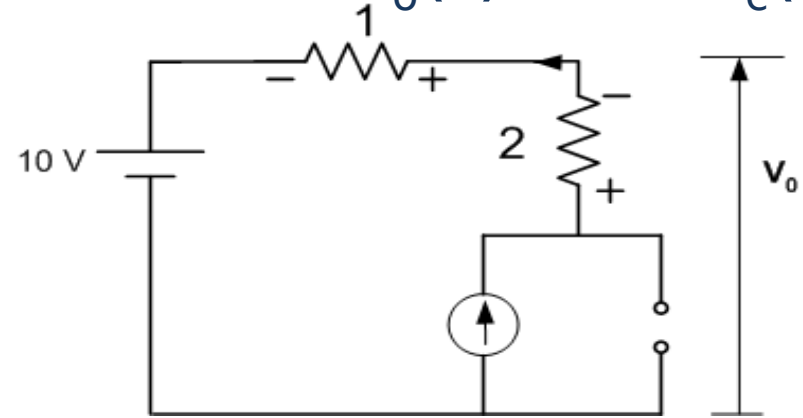b) For $t \geq 0$, find the expressions for $V_o(t)$ and $V_c(t)$

V_c attains a new value governed by circuit parameters.



Equivalent circuit at steady state

At steady state

$$i_c = 0$$

$$V_o = 10 + 5 \times 1 = 15V$$

$$V_c = 10 + 5 \times 3 = 25V$$

$$\tau = 3msec$$

$$V_c = V_f + (V_{in} - V_f)e^{\frac{-t}{\tau}}$$

$$V_f = 25V, V_{in} = 20$$



$$\therefore V_c = 25 - 5e^{\frac{-t}{\tau}}$$

$$V_o = V_c - \frac{(V_c - 10) \times 2}{3} = 15 - \frac{5}{3}e^{\frac{-t}{\tau}}$$



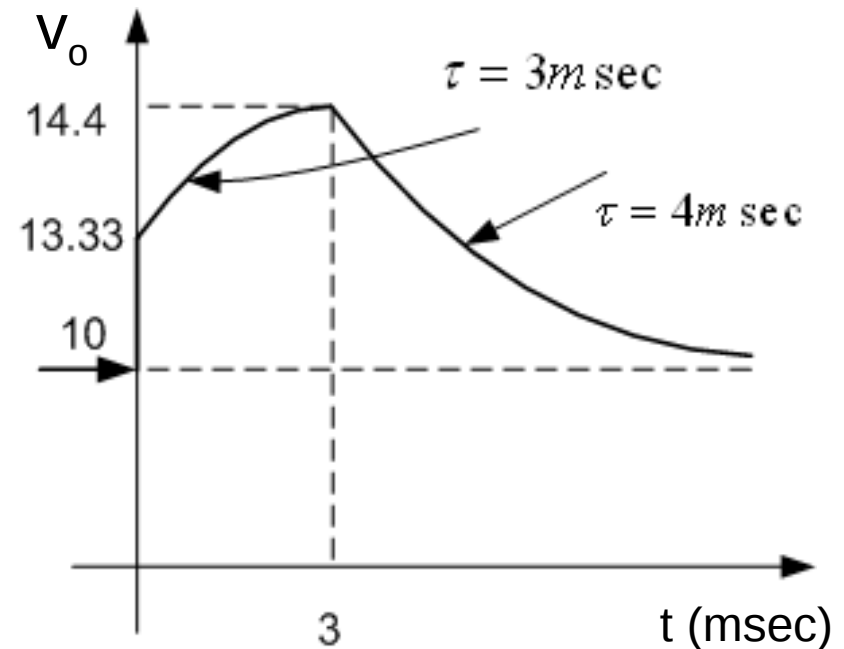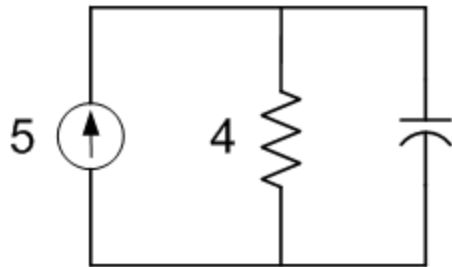c) 'S' is again opened at $t = 3\text{msec}$ sketch V_o for $0 \leq t \leq 10\text{msec}$

At $t = 3\text{msec}$, $V_o = 14.4\text{V}$. When S is opened equivalent circuit is



$V_o \rightarrow 10$ with $\tau = 4\text{msec}$

